

# EEE 202 CIRCUIT THEORY

## LAB 1

### Quality Factor of an Inductor

Design at least two methods to measure the inductance and the quality factor of an inductor at a given frequency.

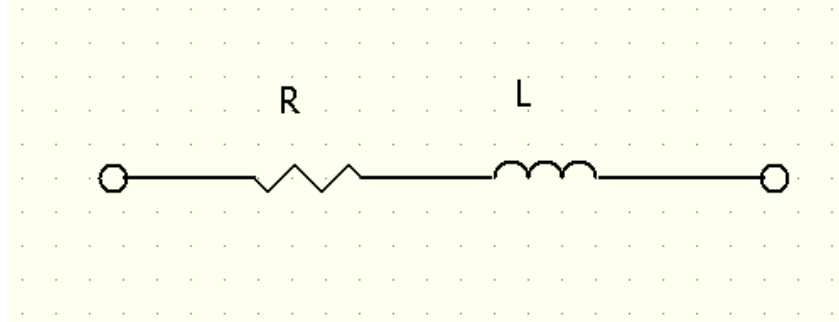


Figure 1: Inductor model using ideal components

As shown in Figure 1 Inductors may be considered as an ideal inductor connected in series with a resistor.  $Q$  of an inductor is defined as:

$$Q = \frac{\omega_0 L}{R} \quad (1)$$

### Preliminary Work

Verify your proposed methods using SPICE.

### Experimental Work

You will use two inductors, one will be provided to you in the lab and you will wind another inductor to a core which will be provided in the lab. Measure the inductance and quality factor of the both inductors using your methods at **four different frequencies** in the range 1MHz to 5MHz, away from self-resonance frequency. Compare your findings. Assess the accuracy of your measurement.

### Available materials in the lab

Toroidal cores to design inductors or transformers: T25-10, T37-7, T38-8, T50-7 from Micrometals. Capacitors with standard values. Resistors with standard values. LM324 (DIP package) Opamp. 10cm x 10cm PCB board pieces with no pattern (just copper on one side) to solder your components.